

Introduction

In this exercise, you will create a verilog implementation of a Finite State Machine (FSM) which corresponds to a **traffic light controller (tlc)**. Assume a crossing where a busy highway crosses a farmroad. There are sensors to detect the presence of cars waiting on the farm road. The traffic light controller has the following properties:


- With no car on the farmroad, light remains green in the highway direction.
- If sensors detect a vehicle on the farmroad, the highway lights go from **green** to **yellow** to **red**, allowing the farmroad lights to become **green**.
- The farm road lights stay **green** only as long as a farmroad car is detected but never longer than a fixed interval of **10 cycles**.
- After this, the farmroad lights transition from **green** to **yellow** to **red**, allowing the highway to return to **green**.
- Even if farmroad vehicles are waiting, highway gets at least a fixed interval of **10 cycles** as **green**.

Important Points:

Assume: Short interval of yellow light = 5 cycles

Maximum interval for green light on the farm road and minimum interval for green on highway = 10 cycles

 The top level block diagram of the traffic light controller system is shown below:




As shown in the diagram above, the traffic light controller system consists of a FSM module named **tlc** and a timer module named **timer**. A module named **tlc_top** wraps these two modules. The details of the signals are given below:

- **detect (1 bit)** - sensor output detecting the presence of a car on the farm road
- **trL(1 bit)** - trigger signal to start counting for **lvalue** cycles

- **trS (1 bit)** - trigger signal to start counting for **svalue** cycles
- **tL (1 bit)** - signal indicating expiration of a time interval of **lvalue** cycles
- **tS (1 bit)** - signal indicating expiration of a time interval of **svalue** cycles
- **state_display (3 bits)**- current state of the FSM module **tlc**
- **hg (1bit)** - highway green
- **hy (1bit)** - highway yellow
- **hr (1bit)** - highway red
- **fg (1bit)** - farm green
- **fy (1bit)** - farm yellow
- **fr (1bit)** - farm red

Assignment

In this assignment, you have to write the FSM module named **tlc**. It takes input signals **clk**, **reset**, **detect**, **tL**, **tS** and output signals **hg**, **hy**, **hr**, **fg**, **fy**, **fr**, **state_display**. **trL**, **trS**. Assume all input and output signals to be 1 bit wide except **state_display** which is 3 bits wide and little endian. The **state_display** must output the number of the current state using the same numbers as the states in the FSM diagram above (shown in red). The **reset** input always makes a transition to the **START** state. The **reset** output is a **synchronous** signal (i.e. it goes high only at posedge of clock). The state transition diagram for the FSM module is given below:

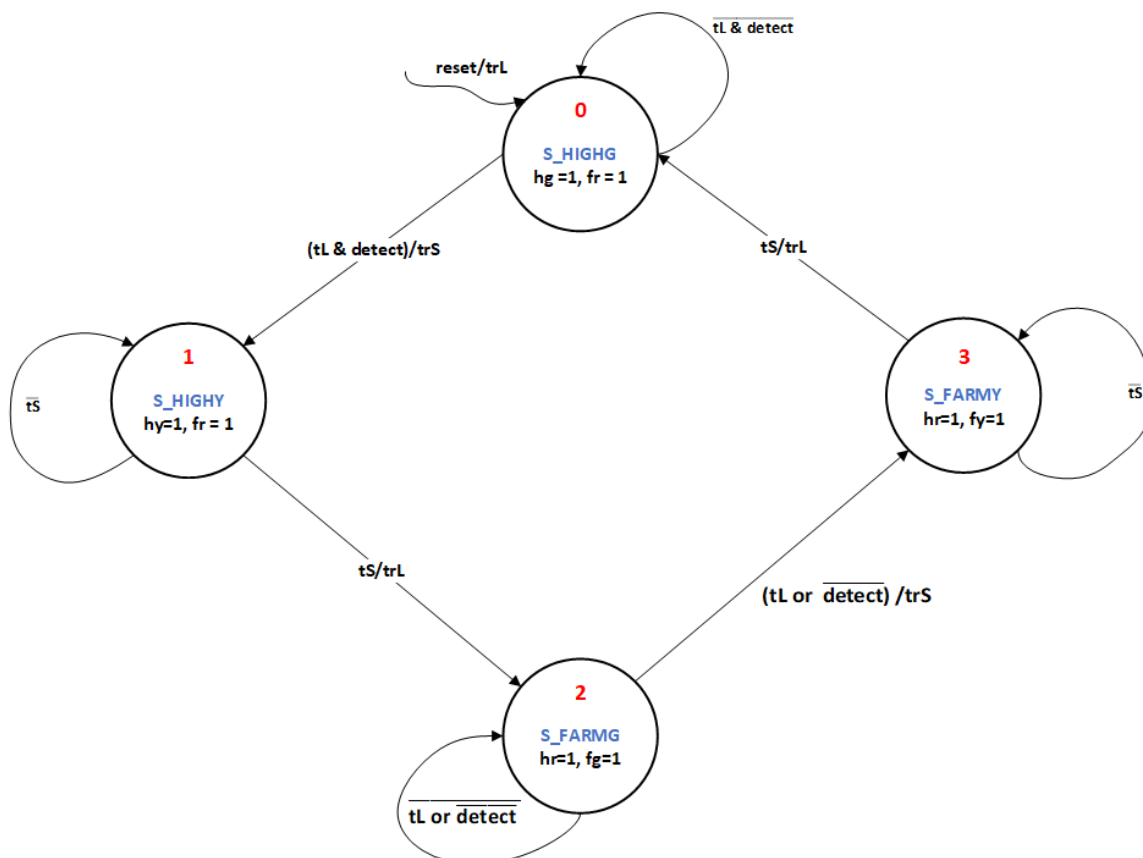

Note: The **timer** module is already provided. The **timer** module synchronizes with the **tlc** module using **tL** and **tS** signals. Configure the parameters **svalue** and **lvalue** as per the design of your **tlc** module to obtain the following behaviour:

- A delay of 10 cycles while transitioning from state 0 to state 1.

- A delay of 5 cycles while transitioning from state 1 to state 2.
- A delay of 10 cycles while transitioning from state 2 to state 3.
- A delay of 5 cycles while transitioning from state 3 to state 0.

Use the template given below for designing the FSM:

```

• `timescale 1ns / 1ps
•
• module tlc(clk, reset, detect, hg, hy, hr, fg, fy, fr, tL, tS, state_display, trL, trS);
•     <<Write your FSM logic here>>
• endmodule
•
• module tlc_top(clk,reset,detect, hg, hy, hr, fg, fy, fr, state_display);
•     input clk, reset, detect;
•     output hg, hy, hr, fg, fy, fr;
•     output [2:0] state_display;
•     wire trL, trS, tL, tS;
•
•     parameter svalue = <<Change svalue to make tS=5 cycles>>;
•     parameter lvalue = <<Change lvalue to make tL=10 cycles>>;
•
•     timer #(
•         .svalue(svalue),
•         .lvalue(lvalue))
•     timer_inst(
•         .clk(clk),
•         .reset(reset),
•         .trL(trL),
•         .trS(trS),
•         .tL(tL),
•         .tS(tS));
•
•     tlc tlc_inst(
•         .clk(clk),
•         .reset(reset),
•         .detect(detect),
•         .hg(hg),
•         .hy(hy),
•         .hr(hr),
•         .fg(fg),
•         .fy(fy),
•         .fr(fr),
•         .trL(trL),
•         .trS(trS),

```

```
• .tL(tL),  
• .tS(tS),  
• .state_display(state_display));  
•  
• endmodule
```