

Computation II: embedded system design (5EIB0)

Description

Submission view



Part 2e: 2020-04-16 Finite State Machine (Design a Parameterized Timer - 7pt)

Available from: Thursday, 16 April 2020, 3:35 PM


Due date: Thursday, 16 April 2020, 5:30 PM

Requested files: timer.v (Download)

Type of work: Individual work

Assignment

 In this assignment, you will create a verilog implementation of a **timer**. The timer is able to count two different timing intervals based on the trigger inputs. You can count for a shorter timing interval and a longer timing interval. These timing intervals are parameterized. The top level diagram of the timer is shown below:



As shown in the diagram above, the timer module has the following signals:

- **clk (1 bit)**
- **reset(1 bit)**
- **trS (1 bit)** - trigger signal to start counting for **svalue** cycles
- **trL (1 bit)** - trigger signal to start counting for **lvalue** cycles
- **tL (1 bit)** - signal indicating expiration of a time interval of **lvalue** cycles
- **tS (1 bit)** - signal indicating expiration of a time interval of **svalue** cycles


Important Points:

- 1) "svalue" and "lvalue" are input parameters;
They determine the shorter and the longer timing intervals respectively.
- 2) Input signals "trS" and "trL" cannot be high at the same time.
- 3) Output signals "tS" and "tL" cannot be active at the same time.

Timing behaviour of Timer:

 - 1) **trL = 1, trS = 0:** Make **tL = 1** after **lvalue** cycles.
- 2) **trL = 0, trS = 1:** Make **tS = 1** after **svalue** cycles.
- 3) **trL = 0, trS = 0:** No change

Timing behaviour of the timer for **svalue = 2 cycles** and **lvalue = 5 cycles** is shown below:



Note: The **reset** is a **synchronous** signal (i.e. it goes high only at posedge of clock). Also, make all transitions at the posedge of **clk**. **Make sure the maximum possible time interval for which the timer can count is greater than 500 cycles.**

Use the template given below for designing the timer:

```
`timescale 1ns / 1ps
module timer(clk,reset, trL, trS, tL, tS);
    input clk, reset, trL, trS;
    output tL, tS;


    parameter svalue = <<svalue>>;
    parameter lvalue = <<lvalue>>;

    <<Logic for timer>>

endmodule
```

Debug

 Click on the symbol marked below to see the waveforms produced by your design. Please note that if your code has an error that prevents it being simulated it will not produce any waveforms.



Requested files

timer.v

```
1 `timescale 1ns / 1ps
2 module timer(clk,reset, trL, trS, tL, tS);
3     input clk, reset, trL, trS;
4     output tL, tS;
5
6     parameter svalue = <<svalue>>;
7     parameter lvalue = <<lvalue>>;
8
9     <<Logic for timer>>
10
11 endmodule
```

[Return to: Final Exam 2020... ➡](#)